

values of IC_0 . The output voltage is always *larger* than the input voltage, but the difference becomes very small for $I_1 \gg I_b$. For a given value of I_1/I_b , the difference is minimum if $IC_0 \ll 1$ (OTA without feedback in weak inversion).

A high current efficiency can be obtained by choosing $B \gg 1$ (ratio of mirror M_3 - M_7).

As long as the differential pair remains in weak inversion, (8.25) reduces to

$$\frac{V_i - V_o}{nU_T} = -\ln\left(1 + \frac{I_b}{I_1}\right). \quad (8.26)$$

8.4 Exponential Characteristics

8.4.1 Voltage and Current Reference

The exponential dependency of the drain current on V_S/U_T makes it possible to extract a voltage proportional to U_T as shown in Figure 8.8. The basic

 


Fig. 8.8. Voltage and current reference: (a) basic circuit; (b) resistor-less current reference.

circuit [31] shown in part (a) of the figure contains a 1-to- K N-channel current mirror M_1 - M_2 , with the source of M_2 degenerated by a resistor R . A 1-to-1 P-channel current mirror M_3 - M_4 (or any equivalent circuit) imposes the same current in the two branches. Therefore, a source voltage V_R builds-up across resistor R to compensate the ratio K of the N-channel mirror. If this mirror is in weak inversion, then

$$V_R = RI = U_T \ln K. \quad (8.27)$$

This voltage should be sufficiently larger than the threshold mismatch of M_1 - M_2 . In practice, it cannot be made much larger than $4U_T$, which corresponds to $K = 55$. It can be used as a PTAT voltage reference, or as a compensation voltage in a band gap voltage references [32].

A reference current I can be extracted by the additional mirror transistor M_5 . Thanks to the small value of V_R a small current can be obtained with a reasonably low value of R .

If the transistor M_2 is in a separate well connected to its source, as shown by the dotted line, then $V_{S2} = V_{S1} = 0$. The factor K is then compensated by a difference of gate voltages, and U_T is multiplied by n in (8.27).

Figure 8.8(b) shows a variant of the basic circuit in which the resistor is replaced by transistor M_6 [166]. This transistor is the output transistor of a current mirror M_7 - M_6 of ratio 1 to A , that operates in *strong inversion*, with the reference current itself as its input. If $A \gg 1$, then $I_{F6} = AI_{F7} = AI \gg I$. Hence, far from being saturated, M_6 is biased close to $V_D = V_S = 0$ where it behaves like a resistor of value $R = 1/G_{ms6}$ given by (5.45):

$$1/R = G_{ms6} = \sqrt{2n\beta_6 AI}. \quad (8.28)$$

By introducing this value in (8.27) we obtain, after arranging the result

$$I = 2n\beta_6 U_T^2 \cdot A(\ln K)^2 = I_{spec6} \cdot A(\ln K)^2. \quad (8.29)$$

This current is obtained without using any resistor, and is proportional to the specific current of transistor M_6 . Therefore, as noticed at the end of Section 5.7, it becomes almost independent of the temperature if the mobility is proportional to $T^{-\alpha}$ with $\alpha \cong 2$.

In practice, (8.28) is an acceptable approximation for $A > 5$.

It should be mentioned that the loop M_6 - M_2 - M_4 - M_8 - M_7 implements a positive feedback. However, the gain of this loop can be shown to be $1/2$ at equilibrium.

8.4.2 Amplitude Regulator

The exponential characteristics of transistors in weak inversion are exploited in the amplitude regulator depicted in Figure 8.9(a) [31]. The sinusoidal signal of amplitude V produced by the oscillator enters the regulator through capacitor C_1 , and transistor M_5 delivers the output current used to bias the oscillator.

When no oscillation is present ($V = 0$), the circuit is reduced to the current

 


Fig. 8.9. Amplitude regulator for oscillators: (a) circuit; (b) transfer characteristics.

reference of Figure 8.8(a). According to (8.27), it delivers an output current

$$I = I_0 = BU_T \ln K/R_3, \quad (8.30)$$

which serves as the start-up current of the oscillator. As the oscillation voltage grows, it is superimposed on the DC component of gate voltages V_{Gdc} for M_1 , but not for M_2 , since it is blocked by the low-pass filter R_2 - C_2 . Because of the exponential function $I_D(V_G)$ of M_1 , its average drain current should increase, which is not compatible with the 1-to-1 ratio imposed by the mirror M_4 - M_3 . Instead, V_{Gdc} decreases, resulting in a decrease of the output current I .

Assuming that all transistors remain saturated, that M_1 remains in weak inversion even during the peaks of its drain current, and that the residual oscillation amplitude at the gate of M_2 is much smaller than U_T (so that it has no nonlinear effect), the transfer characteristics are given by [31]

$$I = I_0 \cdot \left(1 - \frac{\ln I_{B0} \left(\frac{V}{nU_T} \right)}{\ln K} \right), \quad (8.31)$$

where I_{B0} is the 0-order modified Bessel function. They are plotted in Figure 8.9(b) for several values of K .

The amplitude of oscillation will stabilize when the regulator delivers exactly the bias current I required to produce the amplitude V .

If the peak drain current of M_1 leaves weak inversion, the transfer characteristics will be modified and may eventually lose their monotonicity, which must absolutely be avoided to maintain stable oscillation. A semi-empirical condition to ensure monotonicity is

$$\beta_1 > \frac{2\beta_3/\beta_4}{nU_T R_3}. \quad (8.32)$$

The role of capacitor C_3 is to keep the drain voltage of M_1 sufficiently constant to avoid de-saturation during the positive peaks of current.

At low frequencies, high (non-critical) values may be needed for resistors R_1 and R_2 . Very high values have been obtained by using lateral diodes in the polysilicon layer [167, 37]. Lower values can be obtained by means of transistors adequately biased [46].

This amplitude regulator has been applied extensively to quartz oscillators in watches [37, 46, 168, 169, 170], but it can be used in different type of sinusoidal oscillators as well [38].

8.4.3 Translinear Circuits

Discovered for bipolar transistors, the translinear principle [171] is an outstanding application of the exponential characteristics of MOS transistors in weak inversion. Consider the loops of saturated transistors illustrated in Figure 8.10. They include an even number of transistors, half of which have their gate to source "junction" in the clockwise (cw) direction, the other half in the

 


Fig. 8.10. Translinear loops: (a) alternated orientation of transistors in a common substrate; (b) non-alternated orientation: separate local substrates are necessary.

$$\sum_{cw} (V_{Gi} - V_{Si}) = \sum_{ccw} (V_{Gi} - V_{Si}). \quad (8.33)$$

If all transistors are in weak inversion, with negligible reverse current (saturated), then according to (5.41):

$$I_i = I_{D0i} \exp \frac{V_{Gi}/n_i - V_{Si}}{U_T} \quad \text{or} \quad \frac{V_{Gi}}{n_i} - V_{Si} = U_T \ln \frac{I_i}{I_{D0i}}. \quad (8.34)$$

Now if cw and ccw transistors are *alternated* [172] as in Figure 8.10(a), then each gate voltage V_{Gi} is common to a pair cw-ccw of transistors. It appears therefore in both sides of equation (8.33), which can thus be rewritten as

$$\sum_{cw} \left(\frac{V_{Gi}}{n_i} - V_{Si} \right) = \sum_{ccw} \left(\frac{V_{Gi}}{n_i} - V_{Si} \right). \quad (8.35)$$

We can now introduce (8.34), divide by U_T (that is common to all transistors) and exponentiate both sides of the equation, which yields

$$\prod_{cw} \frac{I_i}{I_{D0i}} = \prod_{ccw} \frac{I_i}{I_{D0i}} \quad \text{or} \quad \frac{\prod_{cw} I_i}{\prod_{ccw} I_i} = \frac{\prod_{cw} I_{D0i}}{\prod_{ccw} I_{D0i}} = \lambda. \quad (8.36)$$

This result is independent of the temperature. If I_{D0} is the same for all transistors, then $\lambda = 1$. A circuit may include several loops sharing some transistors, each loop characterized by its value of λ . The mismatch of I_{D0i} is dominated by that of V_{T0i} and results in an error in the value of λ , with a standard deviation

$$\frac{\sigma(\Delta\lambda)}{\lambda} = \frac{1}{nU_T} \left[\sum \frac{1}{2} \sigma^2(\Delta V_{T0i}) \right]^{1/2}, \quad (8.37)$$

where the factor 1/2 comes from the fact that $\sigma(\Delta V_{T0})$ is defined for a pair of transistors.

The current-mode multiplier/divider [173] shown in Figure 8.11(a) is a simple example of a single translinear loop with identical transistors ($\lambda = 1$) of alternated orientations.